

FACULTY OF ELECTRICAL ENGINEERING	
Subject ELECTRICAL ENGINEERING LABORATORY	Review : 6
Subject Code SKEE 2742	Release Date : February 2020
	Last Amendment : March 2023
	Procedure Number : PK-UTM-FKE-(O)-08



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

**FACULTY OF ELECTRICAL ENGINEERING
UNIVERSITI TEKNOLOGI MALAYSIA**

SKEE 2742

ELECTROTECHNIC LABORATORY

EXPERIMENT 3

R-L AND R-C SERIES CIRCUIT TRANSIENT

Disediakan oleh :	Disahkan oleh : Ketua Jabatan
Nama : PM Dr. Md Pauzi Abdullah	Nama : Prof. Madya Ts. Dr. Shahrin
PM Dr. Shahrin Md Ayob	Bin Md Ayob
Dr. Zulkarnain Ahmad Noorden	
Ir. Dr. Syed Norazizul Syed Nasir	
PM Dr. Mohd Junaidi Abdul Aziz	
Dr. Norjulia Mohamad Nordin	
Tandatangan ::	Tandatangan :
Cop :	Cop :
Tarikh :	Tarikh :

FACULTY OF ELECTRICAL ENGINEERING	
Subject ELECTRICAL ENGINEERING LABORATORY	Review : 6
	Release Date : February 2020
	Last Amendment : March 2023
Subject Code SKEE 2742	Procedure Number : PK-UTM-FKE-(O)-08

I. PRELIMINARY EXERCISE (10 marks)

Important Note: Student required to do this exercise BEFORE the lab session.

Part 1: RL Circuit (5 marks)

- i. Explain time constant, τ in circuit analysis.
- ii. The switch in **Figure 1** has been in position ‘a’ for a long time. At $t = 0$, the switch moves to ‘b’.
 - a. Derived an expression of $V_R(t) = V_S e^{-(t/\tau)}$
 - b. If $L = 400$ mH and $V_S = 5$ V,
 - i. Determine $V_R(t)$ at $t = \tau, 2\tau, 3\tau$ and 4τ for R values of 4 k Ω , 6 k Ω and 8 k Ω .
 - ii. Sketch the response of $V_R(t)$ versus t .

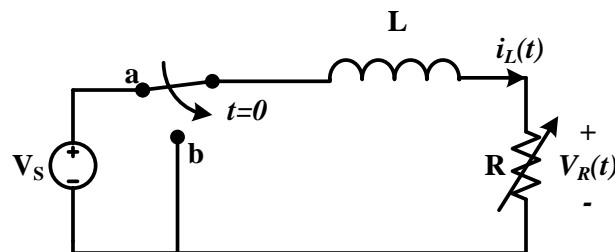


Figure 1

- iii. The switch in **Figure 2** has been in position ‘b’ for a long time. At $t = 0$, the switch moves to ‘a’.
 - a. Derived an expression of $V_R(t) = V_S (1 - e^{-(t/\tau)})$
 - b. If $L = 400$ mH and $V_S = 5$ V,
 - i. Determine $V_R(t)$ at $t = \tau, 2\tau, 3\tau$ and 4τ for R values of 4 k Ω , 6 k Ω and 8 k Ω .
 - ii. Sketch the response of $V_R(t)$ versus t .

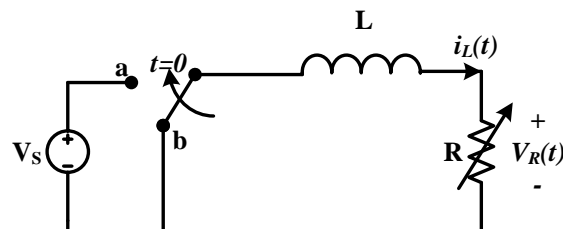


Figure 2

- iv. Suggest experimental procedures (with appropriate software) to prove the result obtained from the exercise using square wave signal generator instead of switch.

FACULTY OF ELECTRICAL ENGINEERING	
Subject ELECTRICAL ENGINEERING LABORATORY	Review : 6
	Release Date : February 2020
	Last Amendment : March 2023
Subject Code SKEE 2742	Procedure Number : PK-UTM-FKE-(O)-08

Important note : Students required to choose and ready with appropriate software (MATLAB, PSPICE, Multism or equivalent). Students must be able to use the software for this experiment.

Part 2: RC Circuit [5 marks]

- i. Explain time constant, τ in circuit analysis.
- ii. The switch in **Figure 3** has been in position ‘a’ for a long time. At $t = 0$, the switch moves to ‘b’.
 - a. Derived an expression of $V_C(t) = V_S e^{-(t/\tau)}$
 - b. If $R = 1 \text{ k}\Omega$ and $V_S = 5 \text{ V}$,
 - i. Determine $V_C(t)$ at $t = \tau, 2\tau, 3\tau$, and 4τ for C values of $0.05 \mu\text{F}$, $0.1 \mu\text{F}$ and $0.15 \mu\text{F}$.
 - ii. Sketch the response of $V_C(t)$ versus t .

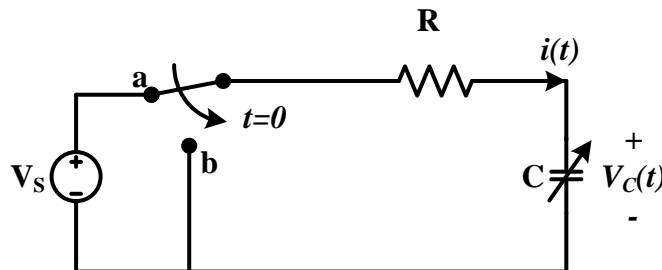


Figure 3

- iii. The switch in **Figure 4** has been in position ‘b’ for a long time. At $t = 0$, the switch moves to ‘a’.
 - a. Derived an expression of $V_C(t) = V_S (1 - e^{-(t/\tau)})$
 - b. If $R = 1 \text{ k}\Omega$ and $V_S = 5 \text{ V}$,
 - i. Determine $V_C(t)$ at $t = \tau, 2\tau, 3\tau$, and 4τ for C values of $0.05 \mu\text{F}$, $0.1 \mu\text{F}$ and $0.15 \mu\text{F}$.
 - ii. Sketch the response of $V_C(t)$ versus t .

FACULTY OF ELECTRICAL ENGINEERING	
Subject ELECTRICAL ENGINEERING LABORATORY	Review : 6
	Release Date : February 2020
	Last Amendment : March 2023
Subject Code SKEE 2742	Procedure Number : PK-UTM-FKE-(O)-08

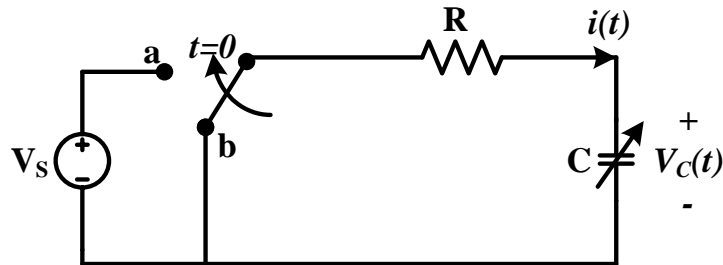


Figure 4

- iv. Suggest experimental procedures (with appropriate software) to prove the result obtained from the exercise using square wave signal generator instead of switch.

Important note : Students required to choose and ready with appropriate software (MATLAB, PSPICE, Multism or equivalent). Students must be able to use the software for this experiment.

FACULTY OF ELECTRICAL ENGINEERING	
Subject ELECTRICAL ENGINEERING LABORATORY	Review : 6
Subject Code SKEE 2742	Release Date : February 2020
	Last Amendment : March 2023
	Procedure Number : PK-UTM-FKE-(O)-08

II. EXPERIMENT

'R-L and R-C Series Transient Circuits'

IMPORTANT: Student need to complete the PRELIMINARY EXERCISE before the laboratory session.

1. Aims:

- i. To investigate the current time response in RL circuit due to changes of resistance.
- ii. To investigate the voltage time response in RC circuit due to changes of capacitance.

2. Instructions:

i. Part 1: RL Circuit

Based on item (iv) in the preliminary exercise (Part 1), perform the RL circuit experiment. Record/draw the results in appropriate table/graph. Find the relationship between the time constant and the voltage response. Compare and discuss the results with preliminary exercise. Perform the experiment using any simulation tools (PSPICE, MATLAB, Multisim, etc.) to validate your results (use a 500 Hz square wave signal for V_s).

ii. Part 2: RC Circuit

Based on item (iv) in the preliminary exercise (Part 2), perform the RC circuit experiment. Record/draw the results in appropriate table/graph. Find the relationship between the time constant and the voltage response. Compare and discuss the results with preliminary exercise. Perform the experiment using any simulation tools (PSPICE, MATLAB, Multisim, etc.) to validate your results (use a 500 Hz square wave signal for V_s).