

| <b>SEKOLAH KEJURUTERAAN ELEKTRIK</b>     |   |
|--|---|
| Nama Matapelajaran: Makmal Tahun 3 (PBL) | Semakan : 3                             |
| Kod Matapelajaran : SKEE 3742            | Tarikh Keluaran : 2008                  |
|  | Pindaan Terakhir : 2019                 |
|  | No. Prosedur : <b>PK-UTM-FKE-(0)-10</b> |



## **SKEE 3742**

**SEKOLAH KEJURUTERAAN ELEKTRIK  
FAKULTI KEJURUTERAAN  
UNIVERSITI TEKNOLOGI MALAYSIA**

# **POWER ELECTRONICS LABORATORY PROBLEM PACK**

## **4-Quadrant DC Motor Drive**

|                              |                          |
|------------------------------|--------------------------|
| Disediakan oleh:             | Disahkan oleh:           |
| PM. Dr. Nik Rumzi Nik Idris  | Pengarah Program         |
| PM. Dr. Nazeera Ahmad Azli   | Dr. Jasrul Jamani Jamian |
| PM. Dr. Awang Jusoh          |                          |
| PM. Dr. Junaidi Abdul Aziz   |                          |
| PM. Dr. Shahrin Md. Ayob     |                          |
| PM. Ir. Dr. Tan Chee Wei     |                          |
| Dr. Mohd. Rodhi Sahid        |                          |
| Dr. Norjulia Mohammad Nordin |                          |
| En. Nik Din Muhammad         |                          |
| En. Zaki Daud                |                          |
| Tarikh : 18 Julai 2019       | Tarikh : 18 Julai 2019   |

**Project Introduction:**

In a modern electrical drive system, the motor is normally fed by a power electronic converter to obtain higher efficiency and flexibility. The task of the converter is to supply the motor with a variable voltage and/or current so that the speed, torque or position of the motor can be controlled with minimum losses. There are several types of power electronic converters that can be used depending on the type of applications in hand. In most of the variable speed drive applications, we are required to control the speed of the motor in either reverse or forward direction. For these types of applications, the so-called 4-quadrant converters are required.

For the next three weeks, you will be studying the four-quadrant converter used in DC motor drive applications. You will need to simulate, construct and test the converter using the available modules in the lab.

Project tasks:

- a) To simulate the 4-quadrant converter using Matlab/SIMULINK
- b) To construct the 4-quadrant converter using the available modules.