

SEKOLAH KEJURUTERAAN ELEKTRIK	
Nama Matapelajaran: Makmal Tahun 3 (PBL)	Semakan : 3
Kod Matapelajaran : SKEE 3742	Tarikh Keluaran : 2008
	Pindaan Terakhir : 2019
	No. Prosedur : PK-UTM-FKE-(0)-10



SKEE 3742

**SEKOLAH KEJURUTERAAN ELEKTRIK
FAKULTI KEJURUTERAAN
UNIVERSITI TEKNOLOGI MALAYSIA**

POWER ELECTRONICS LABORATORY STUDENT PACK


4-quadrant DC Motor Drive

<p>Disediakan oleh:</p> <p>PM. Dr. Nik Rumzi Nik Idris PM. Dr. Naziha Ahmad Azli PM. Dr. Awang Jusoh PM. Dr. Junaidi Abdul Aziz PM. Dr. Shahrin Md. Ayob PM. Ir. Dr. Tan Chee Wei Dr. Mohd. Rodhi Sahid Dr. Norjulia Mohammad Nordin En. Nik Din Muhammad En. Zaki Daud</p> <p>Tarikh : 18 Julai 2019</p>	<p>Disahkan oleh:</p> <p>Pengarah Program Dr. Jasrul Jamani Jamian</p> <p>Tandatangan Cop :</p> <p>Tarikh : 18 Julai 2019</p>
---	---

1

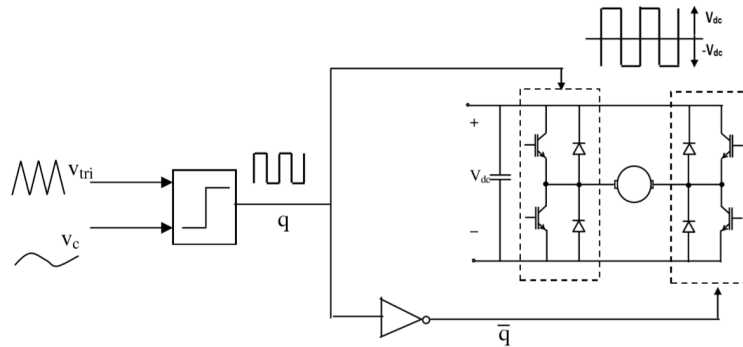Problem/Project Guide:

A 4-quadrant DC-DC converter is used to control the DC motor drives that require forward and reverse motoring as well as forward and reverse braking. The four quadrant converter for DC motor drive which we will study in this lab consists of four power switches (IGBTs with anti-parallel diodes). Figure 1 shows the topology and control of this converter when it is used to feed a DC motor.



Your task is to simulate the 4-quadrant converter and its control using SIMULINK and to show that the converter is indeed capable of operating in all quadrants of operation. You are then required to implement this 4-quadrant converter using the equipment modules available in the lab. The SIMULINK model of the DC motor will be provided to you during the lab session. You should also compare and discuss on the waveforms obtained from the simulation and experiment.

(a) Problem-solving Time-line

Activities	Week 1	Week 2	Week 3
1. Understand the given problem. Identify what you already know and what you need to know. Brainstorming for ideas. Identify the tools that will be used.	✓		
2. Present ideas to facilitator. Start working on solution and simulation design Run the simulation to obtain results.		✓	
3. Set-up hardware and run experiment. Validate the simulation result.			✓

(b) Your report for this laboratory must include:

- Discussion on the basic operation of 4-quadrant converter,
- SIMULINK model and simulation results of the 4-q converter,
- experimental results from oscilloscope,
- Discussions on all the simulation and experimental results

2

Equipments list:

1. DC motor: $R_a = 8\Omega$, $L_a = 3.9\text{mH}$, Back EMF constant = 0.0518 V/rad-1
2. DC generator to be used as a tacho generator (speed sensor)

	<p>3. DC power supply (input DC voltage for the converter): set to 30V</p> <p>4. Modules from the bench:</p> <ul style="list-style-type: none"> a) 4 IGBT switches to construct the 4-quadrant DC-DC converter(735342) b) PWM generator (735341) c) Voltmeter d) Ammeter e) Potentiometer (73402) f) Oscilloscope <p>Please ensure that your circuit is checked by the lab supervisor/facilitator before running the experiment.</p>
3	Components list:
	none
4	Software:
	<ul style="list-style-type: none"> • Matlab/SIMULINK simulation package (installed on PCs in the Power Electronics Lab) • SIMULINK model of the DC motor will be provided to you during the laboratory session.
5	Additional resources:
	You are expected to have the basic knowledge in power electronic DC-DC converter.
6	References
	"Power Electronics: Converters, Applications, and Design - 3rd Ed.", Ned Mohan, Wiley, 2002. (Chapter 7, Section 7.7, "FULL-BRIDGE dc-dc CONVERTER")